

1. (a) The source current( $i_s$ ) and the inductor current( $i_l$ ) for the circuit in Fig. 1(a):

$$i_l = \frac{V_m}{\omega L} [\sin(\omega t + \phi) - \sin(\omega t_o + \phi)] u(t - t_o)$$

$$i_s = \left( \frac{V_m}{R} \cos(\omega t + \phi) + \frac{V_m}{\omega L} [\sin(\omega t + \phi) - \sin(\omega t_o + \phi)] \right) u(t - t_o)$$

- (b) The voltage across the resistor( $V_r$ ) and the inductor current( $i_l$ ) for the circuit in Fig. 1(b):

$$i_l = I_m \sin \omega t u(t - t_o)$$

$$V_r = I_m R \sin \omega t u(t - t_o)$$

- (c) The source current( $i_s$ ) and the capacitor current( $i_c$ ) for the circuit in Fig. 1(c):

**Case 1:** If  $\omega t_o = n\pi$  (or)  $t_o = \frac{n\pi}{\omega}$

$$i_c = CV_m \omega \cos \omega t u(t - t_o)$$

$$i_s = [CV_m \omega \cos \omega t + \frac{V_m}{R} \sin \omega t] u(t - t_o)$$

**Case 2:** If  $\omega t_o \neq n\pi$  (or)  $t_o \neq \frac{n\pi}{\omega}$

$$i_c = CV_m [\omega \cos \omega t u(t - t_o) + \sin \omega t \delta(t - t_o)]$$

$$i_s = CV_m [\omega \cos \omega t u(t - t_o) + \sin \omega t \delta(t - t_o)] + \frac{V_m \sin \omega t}{R} u(t - t_o)$$

- (d) The voltage across the resistor( $V_r$ ) and the capacitor current( $i_c$ ) for the circuit in Fig. 1(d):

$$i_c = I_m \cos(\omega t + \phi) u(t - t_o)$$

$$V_r = I_m R \cos(\omega t + \phi) u(t - t_o)$$

2. The expression for the load voltage( $V_l(t)$ ), given the op-amp to be in ideal condition:

$$V_l(t) = -\frac{V_m}{\omega RC} [\sin(\omega t + \phi) - \sin(\phi)]$$

3. Impulse response of circuit shown in Fig. 1(a):

$$i(t) = \frac{u(t - t_o)}{L} + \frac{\delta(t - t_o)}{R}$$

As  $t \rightarrow \infty, i(t) \rightarrow \frac{1}{L}$ , which is a constant. Hence, the system is **marginally stable**.

Similarly, the impulse response of circuit shown in Fig. 1(d):

$$V(t) = \frac{u(t - t_o)}{C} + R \delta(t - t_o)$$

As  $t \rightarrow \infty, V(t) \rightarrow \frac{1}{C}$ , which is a constant. Hence, the system is **marginally stable**.

4. The current through the inductor( $i_l(t)$ ) is:

$$i_l(t) = (t - t_o) e^{-2t} u(t - t_o)$$